

# Full wave rectifier

Mario Sepúlveda-Hernández

February 4, 2025

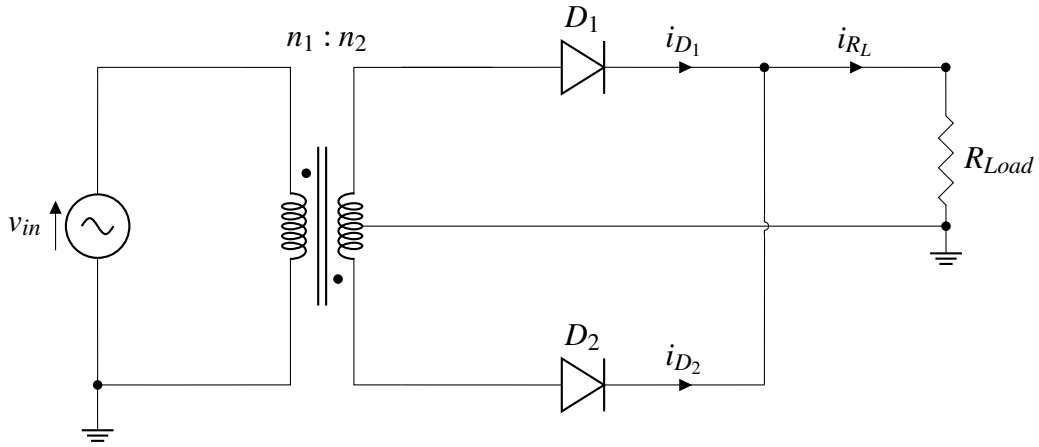


Figure 1: Full-wave rectifier

The Figure 1 is the circuit of a full wave rectifier with 2 diodes where:

$$V_{DC} = \frac{2}{T} \int_0^{\frac{T}{2}} V_m \sin(\omega t) dt = \frac{2V_m}{\pi} = 0.636V_m$$
$$V_{RMS} = \left[ \frac{2}{T} \int_0^{\frac{T}{2}} V_m \sin(\omega t) dt \right]^{\frac{1}{2}} = \frac{V_m}{\sqrt{2}} = 0.707V_m$$