

Inverter configuration

Mario Sepúlveda-Hernández

February 6, 2025

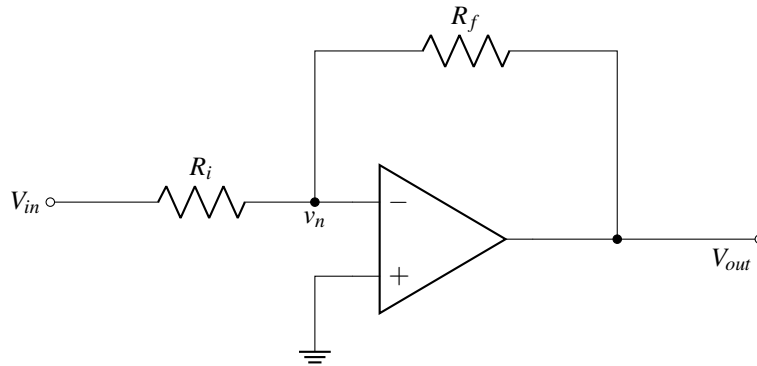


Figure 1: Operational Amplifier (inverter configuration)

The Figure 1 represents the inverter configuration with an operational amplifier; the input signal V_{in} will be inverted at the output V_{out}

$$\begin{aligned}i_i &= i_{in} + i_f \\Z_i &\longrightarrow \infty \implies i_{in} = 0 \\i_i &= i_f \\i_i &= \frac{V_{in} - \overset{0}{v_n}}{R_i} = \frac{V_{in}}{R_i} \\i_f &= \frac{\overset{0}{v_n} - V_{out}}{R_f} = -\frac{V_{out}}{R_f} \\\implies \frac{V_{in}}{R_i} &= -\frac{V_{out}}{R_f} \\\implies \frac{V_{out}}{V_{in}} &= -\frac{R_f}{R_i} = A_v\end{aligned}$$